



W10 Mar 18 (D2) Hardware implementation of C statements

[Jose Ferreira](#)

[All Sections](#)

These questions are presented under the following assumptions:

- They may be selected to be part of the final exam
- Responses must be posted by the students (not me)
- I will call your attention to any mistakes or wrong content posted in response

N.B.: The source of this question is Patrick R. Schaumont, “[A Practical Introduction to Hardware/Software Codesign](#)”, Problem 1.4, pp. 28-29.

Describe a possible implementation for each of the following C statements in hardware (use a block diagram). You can assume that all variables are integers, and that each of them is stored in a register.

1. $a = a + 1$;
2. if ($a > 20$) $a = 20$;
3. while ($a < 20$) $a = a + 1$;

